

# Contents

0.1	How can I print off and use this document? . . . . .	ii
0.2	How to contribute to GitHub . . . . .	iii
0.3	Who comprises this class and how can they be reached? . . .	iv
0.3.1	The Captain at the helm . . . . .	iv
0.3.2	The A-Team . . . . .	iv
0.3.3	You, yourselves . . . . .	iv
0.4	The policies of this class . . . . .	v
<b>I</b>	<b>Circuits</b>	<b>1</b>
<b>1</b>	<b>I. Potential, current, energy, conservation</b>	<b>3</b>
1.1	What is electricity? . . . . .	3
1.2	Charge . . . . .	3
1.3	Current . . . . .	4
1.3.1	The directionality of current . . . . .	4
1.3.2	The at times deadly serious nature of current . . . . .	5
1.3.3	The “speed” of current . . . . .	5
1.4	Potential (difference) . . . . .	6
1.5	Power . . . . .	6
1.6	Energy . . . . .	7
1.7	Conservation . . . . .	7
1.8	Worksheet . . . . .	8
1.8.1	Problem 1, constant charge through a cross-section . .	8
1.8.2	Problem 2, arbitrary charge through a cross-section .	8
1.8.3	Problem 3, a ”tera”ble puzzle . . . . .	8
1.8.4	Problem 4, power necessary to run a pacemaker . . . .	8
1.8.5	Problem 5, energy needed to excite a neuron . . . . .	8
1.8.6	Problem 6, a thump to the chest . . . . .	9

<b>2</b>	<b>II. Circuit elements</b>	<b>11</b>
2.1	Active v. passive . . . . .	11
2.2	Ohm's Law and what it means . . . . .	11
2.3	Sources . . . . .	12
2.4	Resistors . . . . .	12
2.4.1	Resistance, $R$ . . . . .	12
2.4.2	Resistivity, $\rho$ . . . . .	12
2.4.3	Resistance, $R$ . . . . .	14
2.4.4	Conductance . . . . .	14
2.5	Capacitors . . . . .	14
2.5.1	Its time varying behavior . . . . .	14
2.5.2	Charge accumulation . . . . .	14
2.5.3	A simple example . . . . .	14
2.6	Inductors . . . . .	14
2.7	Impedance . . . . .	14
2.7.1	A quick note on "imaginary" numbers . . . . .	14
2.8	Equivalent impedance . . . . .	14
2.8.1	Impedances in general . . . . .	14
2.8.2	Resistors . . . . .	14
2.8.3	Capacitors . . . . .	14
2.8.4	Delta-Wye ( $\Delta$ - $Y$ ) transformations . . . . .	14
2.8.5	A few examples . . . . .	14
2.9	Grounds . . . . .	14
2.10	Conductors . . . . .	14
2.11	Operational amplifiers . . . . .	14
2.12	Diodes . . . . .	14
2.13	Switches . . . . .	14
2.14	Transistors . . . . .	14
2.15	Transformers . . . . .	14
2.16	Worksheet . . . . .	15
2.16.1	Problem 1, expressing power in ohms . . . . .	15
2.16.2	Problem 2, a couple toaster based problems . . . . .	15
2.16.3	Problem 3, currently conducting power . . . . .	15
2.16.4	Problem 4, conductance of a sodium channel . . . . .	15
2.16.5	Problem 5, resistance of a simple tissue . . . . .	15
<b>3</b>	<b>III. Operational amplifiers</b>	<b>17</b>
3.1	Some details . . . . .	17
3.2	Some rules . . . . .	17
3.3	Some conveniences . . . . .	17

3.4	Some examples . . . . .	17
3.4.1	Inverting amplifier . . . . .	17
3.4.2	Non-inverting amplifier . . . . .	17
3.4.3	Voltage follower . . . . .	17
3.4.4	Summing amplifier . . . . .	17
3.4.5	Differential amplifier (as homework) . . . . .	17
<b>4</b>	<b>Circuit analysis: I. Nodal analysis</b>	<b>19</b>
4.1	Nodes and branches . . . . .	19
4.2	Kirchhoff's Laws . . . . .	19
4.2.1	Kirchhoff's Current Law . . . . .	19
4.2.2	Kirchhoff's Voltage Law . . . . .	19
4.3	Nodal analysis . . . . .	19
4.4	Solving simultaneous equations . . . . .	19
4.4.1	Cramer's Rule . . . . .	19
<b>5</b>	<b>Circuit analysis: II. Mesh analysis; Homework I</b>	<b>21</b>
5.1	Mesh analysis . . . . .	21
5.2	Steps of mesh analysis . . . . .	21
5.3	Writing mesh equations directly in matrix form . . . . .	21
<b>6</b>	<b>Circuit analysis: III. Supernodes and supermeshes</b>	<b>23</b>
6.1	Nodal analysis with an independent current source . . . . .	23
6.2	Nodal analysis with voltage sources, <b>Supernodes</b> . . . . .	23
6.3	Nodal analysis with controlled sources . . . . .	23
6.4	Mesh analysis with current sources . . . . .	23
6.5	Mesh analysis with controlled sources, <b>Supermeshes</b> . . . . .	23
<b>7</b>	<b>Circuit analysis: IV. Circuit theorems</b>	<b>25</b>
7.1	Circuit theorems . . . . .	25
7.2	Linearity . . . . .	25
7.3	Superposition . . . . .	25
7.4	Source transformation . . . . .	25
7.5	Thevenin equivalents . . . . .	25
7.6	Norton equivalents . . . . .	25
7.7	Equivalents with dependents . . . . .	25
<b>8</b>	<b>Circuit analysis: V. When to choose between analyses</b>	<b>27</b>
<b>9</b>	<b>A review of the material thus far; Homework II</b>	<b>29</b>
9.1	How to measure voltage and current . . . . .	29

<b>II</b>	<b>Systems</b>	<b>33</b>
<b>10</b>	<b>The Laplace Transform: I. What it is and why it is important</b>	<b>35</b>
10.1	How do we know our world looks like this? . . . . .	36
10.2	Euler's identity / Euler's formula . . . . .	36
10.3	The Laplace transform . . . . .	36
10.4	The Laplace transform of 1 . . . . .	36
10.5	The $s$ -plane . . . . .	36
10.6	The linearity of the Laplace transform . . . . .	36
10.7	The Laplace transform of $e^{at}$ . . . . .	36
10.8	The Laplace transform of $dx/dt$ . . . . .	36
10.9	The Laplace transform in RLC circuits . . . . .	36
10.9.1	Resistors . . . . .	36
10.9.2	Inductors . . . . .	36
10.9.3	Capacitors . . . . .	36
10.9.4	RLC . . . . .	36
10.10	Two important places, zeros and poles . . . . .	36
<b>11</b>	<b>The Laplace Transform: II. How to use it</b>	<b>37</b>
11.1	The inverse Laplace transform . . . . .	37
11.2	The Laplace transform of $\sin$ . . . . .	37
11.3	The Laplace transform of $t^n$ . . . . .	37
11.4	Some applicability . . . . .	37
<b>12</b>	<b>Circuits as ODEs: I. First-order</b>	<b>39</b>
12.1	Source-free RC circuits . . . . .	39
12.1.1	One resistor, one capacitor . . . . .	39
12.1.2	Two or more resistors and/or capacitors . . . . .	39
12.2	Source-free "active" circuits . . . . .	39
12.3	First-order systems with sources . . . . .	39
12.4	Several singular functions . . . . .	39
12.4.1	Unit step function, $u(t - t_0) = 1, t > t_0$ . . . . .	39
12.4.2	Unit impulse function, $\delta(t) = du(t)/dt$ . . . . .	39
12.4.3	Unit ramp function, $r(t) = \int u(t)dt$ . . . . .	39
<b>13</b>	<b>Circuits as ODEs: II. Second-order</b>	<b>41</b>
13.1	A series RLC circuit . . . . .	41

<b>14 System response: I. Convolution; Homework III</b>	<b>43</b>
14.1 An introduction to thinking in systems . . . . .	43
14.1.1 Domains of interest, of command . . . . .	43
14.1.2 The time-domain, or: our typical realm . . . . .	43
14.1.3 The frequency-domain, or: our new realm . . . . .	43
14.1.4 The $s$ -domain, or: our magical realm . . . . .	43
14.2 Inputs and outputs . . . . .	43
14.3 Somewhere in the between . . . . .	43
14.4 Convolution in the time-domain . . . . .	43
14.5 Multiplication in the frequency- and $s$ -domain . . . . .	43
<b>15 System response: II. Stability</b>	<b>45</b>
15.1 An introduction . . . . .	45
15.1.1 What do we mean by stability? . . . . .	45
15.2 Undamped, $\zeta = 0$ . . . . .	45
15.3 Underdamped, $0 < \zeta < 1$ . . . . .	45
15.4 Overdamped, $\zeta > 1$ . . . . .	45
<b>III &amp; Signals</b>	<b>47</b>
<b>16 System response: III. The frequency domain</b>	<b>49</b>
<b>17 System response: IV. Filters</b>	<b>51</b>
<b>18 System response: V. Feedback; Homework IV</b>	<b>53</b>
<b>IV in Biomedical Engineering</b>	<b>57</b>
<b>19 Bioelectricity: I. Passive properties</b>	<b>59</b>
19.1 Modeling biological material with a simple circuit, $R_1 + (R_2    C)$	59
19.2 Resistance-Reactance Plane . . . . .	59
19.3 What can we do with this information? . . . . .	59
<b>20 Bioelectricity: II. Active properties</b>	<b>61</b>
<b>21 Bioelectricity: III. Measurement</b>	<b>63</b>
<b>22 Digital circuits: I. Discretization</b>	<b>65</b>
<b>23 Digital circuits: II. Logic; Homework V</b>	<b>67</b>

<b>24 Happenstance: A few BME specific situations</b>	<b>69</b>
<b>25 Circumstance: A few BME specific standards</b>	<b>71</b>
<b>26 A philosophy of circuits, systems, and signals; Homework VI</b>	<b>73</b>

## 0.1 How can I print off and use this document?

Frankly, in just about any way thats useful to you. I am going to try something here, where I will try to make more or less the entirety of the notes associated with the Winter 2019 semester of BIOMEDE 211, Circuits, Systems, and Signals in Biomedical Engineering, to you, dear reader.

Please dont plagiarize this. If you were raised right, you ought to know what that is. If youd like my judgment on any sort of action, my opinions can be laid bare.

The first assignment I am giving you (worth 4% of your grade and which must be completed by the end of the semester) is to figure out where this document is located online, download it, print it off, sign your name to it, and get it to me. If you know who I am, I would expect a competent engineer to find that without much to-do about it. Start with Google, go from there. Further, for those in the class, BIOMEDE 211, Winter 2019, you must join Github and make at least four substantive contributions to this repository. The term all you engineers (and lawyers) cant wait to parse is substantive to which I will always enter a judgment which I deem final in this class, and I am ever in favor of beneficence over stricture. So, just help out the class in a way you think is helpful and watch those around you do the same. Failure to contribute to this living document by the end of the semester for those in this class will result in a loss of up to 4% of one's total grade outright.

## 0.2 How to contribute to GitHub

Follow these general steps to propose a change to this online document:

1. Create a GitHub account

This should be rather self-explanatory. Use your e-mail account and verify it to be able to edit. You should proceed with the following steps while logged onto your account.

2. Find Dr. Belmont's GitHub page and go to the biomed-211-w19 repository ("repo"). Then click on the biomed-211-w19.tex file.

3. Edit the file

You will find a small pencil icon on the right side of the page. Click on this to create your own branch ("forking"), and edit the file as you wish.

4. Propose file change

After making your changes, you should scroll to the bottom of the page, find the message box that says, 'Propose file change', and fill it out. The first line should say what you have updated and can be explained in the description.

5. Create pull request

After finishing your file, you will be brought to a page that displays what you have modified on the original document. Press the green 'Create pull request' button to let Dr. Belmont know that you want to create a change. Once he has approved via his own GitHub account, your changes should now be in the updated master branch!



## **0.3 Who comprises this class and how can they be reached?**

### **0.3.1 The Captain at the helm**

Barry Belmont  
Wednesdays 11:00 a.m. — 1:00 p.m., 2130 LBME  
belmont@umich.edu

### **0.3.2 The A-Team**

Annabelle St. Pierre  
Wednesdays 5:00 p.m. — 6:30 p.m., UGLI basement  
astpierr@umich.edu

Alice Tracey  
Wednesdays 4:00 p.m. — 5:00 p.m., UGLI basement  
atracey@umich.edu

### **0.3.3 You, yourselves**

In this class, we will be learning a lot from each other. You are encouraged to learn from one another. You are encouraged to talk to one another. You are encouraged to share ideas and at times data. You are not encouraged and are hereby expressly forbidden to submit the work of another as your own. If you get help from others, you will put their name on it somewhere. Too much of this and you are committing plagiarism, not enough and you are committing fraud. Please be honest and let's all learn together.

## 0.4 The policies of this class

**Part I**

**Circuits**



# Chapter 1

## I. Potential, current, energy, conservation

01/10/2019

### Contents

---

<b>1.1</b>	<b>What is electricity?</b>	<b>3</b>
<b>1.2</b>	<b>Charge</b>	<b>3</b>
<b>1.3</b>	<b>Current</b>	<b>4</b>
1.3.1	The directionality of current	4
1.3.2	The at times deadly serious nature of current	5
1.3.3	The “speed” of current	5
<b>1.4</b>	<b>Potential (difference)</b>	<b>6</b>
<b>1.5</b>	<b>Power</b>	<b>6</b>
<b>1.6</b>	<b>Energy</b>	<b>7</b>
<b>1.7</b>	<b>Conservation</b>	<b>7</b>
<b>1.8</b>	<b>Worksheet</b>	<b>8</b>
1.8.1	Problem 1, constant charge through a cross-section	8
1.8.2	Problem 2, arbitrary charge through a cross-section	8
1.8.3	Problem 3, a ”tera”ble puzzle	8
1.8.4	Problem 4, power necessary to run a pacemaker	8
1.8.5	Problem 5, energy needed to excite a neuron	8
1.8.6	Problem 6, a thump to the chest	9

---

## 1.1 What is electricity?

- 1.
- 2.
- 3.

## 1.2 Charge

1. Charge is the property of matter that causes it to experience a force when placed in an electromagnetic field; measured in coulombs (C)
- 2.
3. **How many electrons are needed to form one coulomb?** (What is the weight of all those electrons?)
4. One byte is eight bits. Bits are essentially a single electron stored in a transistor. **If we were to take all the electrons from one terabyte of well distributed information (equal number of ones and zeros), how many coulombs would we have?**

## 1.3 Current

1. The time rate of charge (charged particles) in motion; measured in amperes (A); defined mathematically as

$$i := dq/dt \tag{1.1}$$

where  $i$  is current,  $q$  is charge, and  $t$  is time

2. Conversely, the total charge transferred over time can be expressed as

$$Q := \int_{t_0}^t i dt \tag{1.2}$$

3. 1 ampere is equal to 1 coulomb/second
4. Direct current, “DC”
5. Alternative current, “AC”

### 1.3.1 The directionality of current

Ultimately, the direction in which we say "current" flows is largely arbitrary. As arbitrary as choosing one type of charge and calling it "positive" and another "negative". The reason it doesn't matter is that the only consequence of having chosen a "wrong direction" for the current in a given analysis is that we have to switch the sign of the value. Thus, 3 amps in one direction is *the exact same thing* as -3 in the opposite direction.

1. Thanks to Benjamin Franklin we say that current is
  - i. **Positive in the direction in which positively charged particles flow** and
  - ii. **Negative in the direction in which negatively charged particles**
  - iii. We also now know that current results primarily from the movement of negatively charged particles (electrons) and therefore our convention is wrong in one sense, though convenient and entrenched enough that were not liable to change it in our life time (besides, the math comes out the same, and the actual flow of electrons will only matter to us in a few special circumstances, diodes)

### 1.3.2 The at times deadly serious nature of current

Much of the point of learning this material here is its eventual application by our hands or by the hands of those we work with. Before we put any of this stuff in our hands, we should probably know what is and is not safe.

1. 1 mA
2. 10 mA
3. 100 mA
4. 1000 mA

### 1.3.3 The "speed" of current

A possible misconception is that the electrons inside a wire travels at the speed of light. The speed of current is actually relatively slow. If one were to imagine an electron starting at the wire next to a light switch in an average classroom, it would take a very long period of time for it to travel to the light itself. The light's immediate reaction to a switch is due to a "hose

## 6CHAPTER 1. *I. POTENTIAL, CURRENT, ENERGY, CONSERVATION*

effect”; the electrons inside the wire push other electrons in the direction opposite to the [conventional] current. This cascade of electrons is what happens close to the speed of light, not the electron movement itself.



## 1.4 Potential (difference)

1. The amount of work needed to move a unit of (positive) charge from a reference point to another point [without producing an acceleration]).
2. Potential is measured in “volts” and is often called “voltage”. In this class we will endeavor to avoid such a term as it can be very confusing to talk about potential as if there were such a *thing* as voltage.

3. Defined as

$$v := \frac{dw}{dq} \quad (1.3)$$

4. Potential describes the *potential* to do something. Increasing the potential is akin to increasing the height of a cliff. The height does not *do* anything other than increase what can be done on the drop. If potential is the cliff’s height, charge would be pebbles you’d drop off the side, and current describes how fast those pebble fall.
5. In this class, and for the vast vast majority of electrical engineering work, we care about the *difference* in potential. One element held at 100 billion volts and another held at 100 billion + 1 volts has a *potential difference* of 1 V, which is less than a single AA battery.
6. Some typical voltages to be aware of

**Consumer level batteries** (AA, AAA):

**Car batteries:**

**The “mains”** (levels provided by power companies to consumers):

**Power transmission lines:**

## 1.5 Power

1. The time rate of expending or absorbing energy.
2. Quantifies the rate of energy transfer.
3. Mathematically:
4. Measured in watts: 1 W =
5. **Passive sign convention:**

## 1.6 Energy

- 1.
- 2.
- 3.
- 4.

## 1.7 Conservation

Here, as elsewhere, things will be conserved. In electrical circuits there are two laws of conservation that will matter most for us:

1. **The Conservation of Mass.**
2. **The Conservation of Energy.**

In evaluating circuits, the main focus of the first third of this class, it will be the application of these two conservative laws that will enable us to “solve” them. That is, by understanding (1) how energy is generated and used and (2) how charges move around in closed loops (“circuits”) we will be able to predict the behavior of the myriad electrical systems which may cross our paths.

## 1.8 Worksheet

### 1.8.1 Problem 1, constant charge through a cross-section

How much charge passes through a cross-section of a conductor in 60 seconds if a DC current value is measured at 0.1 mA? **Solution**

### 1.8.2 Problem 2, arbitrary charge through a cross-section

Determine the total charge entering a terminal between  $t = 0$  seconds and  $t = 10$  seconds if the current (in amps) passing through is

$$i(t) = \frac{1}{\sqrt{5t + 2}}. \quad (1.4)$$

**Solution**

### 1.8.3 Problem 3, a "tera"ble puzzle

Approximately how much current is necessary to transmit one terabyte of information in an hour? **Solution**

### 1.8.4 Problem 4, power necessary to run a pacemaker

A cardiac pacemaker will provide approximately 5,000 J of energy over 5 years. Determine the capacity of a 5 V lithium battery necessary to drive this pacing such that only 40% of its energy is spent over that time. **Solution**

### 1.8.5 Problem 5, energy needed to excite a neuron

A colleague of yours has been in their lab ginning up new neurons. You, as their resident electrical expert, are tasked with determining the energy consumed by the cell. If the current and voltage variations are found to be functions of time ( $t \geq 0$ )

$$i(t) = 3t \quad (1.5)$$

$$v(t) = 10e^{6t} \quad (1.6)$$

determine the energy consumed between 0 and 2 ms. **Solution**

**1.8.6 Problem 6, a thump to the chest**

(a) A typical defibrillator delivers 200-1000 V in less than 10 ms. How much current is needed to deliver 120, 240, and 360 Joules?

(b) A human heart weighs about 300 grams. From approximately how high of a cliff would one have to drop a heart such that the impact was equivalent to the energy delivered to someone's chest from a defibrillator? **Solution**

# Chapter 2

## II. Circuit elements

01/15/2019

### 2.1 Active v. passive

Active elements are electrical components that can generate their own energy. Examples of active elements would include generators, batteries, and transistors. Due to the fact that they produce energy, active elements are often known as sources. In contrast to this, passive circuit elements do not produce their own energy. Examples of passive elements would be resistors, capacitors, and inductors.

### 2.2 Ohm's Law and what it means

Ohm's Law is concerned with the relationship between voltage, or potential difference, and current across a conductor. The potential difference across a conductor is proportional to the current flowing through the conductor with the proportionality constant being denoted as  $R$ , or resistance. This can be expressed as:

$$V := iR \tag{2.1}$$

This essentially states that the drop in potential across the conductor, or resistor, is equivalent to the current flowing through the conductor and its resistance. When considering impedance, the equation can be modified to state:

$$V := iZ \tag{2.2}$$

## 2.3 Sources

## 2.4 Resistors

Electrical circuit elements that resist the flow of electricity and electric charge  
Passive two terminal element (does not generate its own energy)

### 2.4.1 Resistance, $R$

Resistance =  $R$  and is measured in Ohms  $1 = 1V/1A$  Resistance is the subset of a broad phenomenon known as impedance ( $Z$ ), which is an element's total opposition to a current when a potential is applied.

### 2.4.2 Resistivity, $\rho$

Resistivity: based on 3 parameters

1.  $\rho \rightarrow$  materials ability to resist flow ( $\Omega m$ )
2.  $l \rightarrow$  length of the element (m)
3.  $A \rightarrow$  cross sectional area of element ( $m^2$ )

$$R = \rho \frac{l}{A} \quad (2.3)$$

Resistivity and Materials Materials that exhibit a high resistivity are things that are classified as conductors. Conductors are commonly associated with metals such as silver. In contrast, materials that exhibit a low resistivity are called insulators. Some common examples of insulators would be polymers such as plastics, ceramics and glass.

Here is a link to a video that further explains the concepts of resistivity and resistance: [https://www.youtube.com/watch?v=4rsswT\\_Rv1M](https://www.youtube.com/watch?v=4rsswT_Rv1M).



**2.4.3 Resistance,  $R$** **2.4.4 Conductance****2.5 Capacitors****2.5.1 Its time varying behavior****2.5.2 Charge accumulation****2.5.3 A simple example****2.6 Inductors****2.7 Impedance****2.7.1 A quick note on “imaginary” numbers****2.8 Equivalent impedance****2.8.1 Impedances in general****2.8.2 Resistors****2.8.3 Capacitors****2.8.4 Delta-Wye ( $\Delta$ -Y) transformations****2.8.5 A few examples****2.9 Grounds****2.10 Conductors****2.11 Operational amplifiers****2.12 Diodes****2.13 Switches****2.14 Transistors****2.15 Transformers**



## 2.16 Worksheet

### 2.16.1 Problem 1, expressing power in ohms

Utilizing Ohm's law, express units of power to include ohms.

**Solution**

### 2.16.2 Problem 2, a couple toaster based problems

A toaster draws 2 A at 120 V. What is its resistance?

**Solution**

How much current is drawn by a toaster with a resistance of  $10\ \Omega$  at 110 V?

**Solution**

### 2.16.3 Problem 3, currently conducting power

In the circuit shown, calculate the current,  $i$ , the conductance,  $G$ , and the power,  $p$ .

**Solution**

### 2.16.4 Problem 4, conductance of a sodium channel

Conductance ( $G/A$ ) of a sodium channel of a cell membrane at a specific time is  $10\ \text{mS}/\text{cm}^2$ . If the channel length is 100 nm, what is its conductivity?

**Solution**

### 2.16.5 Problem 5, resistance of a simple tissue

Determine the resistance of a homogenous and isotropic tissue with a cross-sectional area which can be described by the functions  $y = 8 - x^2$  from  $x = -2\ \text{cm}$  to  $x = +2\ \text{cm}$ , a length of 10 cm (parallel to the z-axis), and a resistivity of  $80\ \Omega\text{m}$ .

**Solution**



## Chapter 3

# III. Operational amplifiers

01/17/2019

3.1 Some details

3.2 Some rules

3.3 Some conveniences

3.4 Some examples

3.4.1 Inverting amplifier

3.4.2 Non-inverting amplifier

3.4.3 Voltage follower

3.4.4 Summing amplifier

3.4.5 Differential amplifier (as homework)



## Chapter 4

# Circuit analysis: I. Nodal analysis

01/22/2019

### 4.1 Nodes and branches

### 4.2 Kirchhoff's Laws

#### 4.2.1 Kirchhoff's Current Law

#### 4.2.2 Kirchhoff's Voltage Law

### 4.3 Nodal analysis

### 4.4 Solving simultaneous equations

#### 4.4.1 Cramer's Rule



## Chapter 5

# Circuit analysis: II. Mesh analysis; Homework I

01/24/2019

**5.1 Mesh analysis**

**5.2 Steps of mesh analysis**

**5.3 Writing mesh equations directly in matrix form**





## Chapter 6

# Circuit analysis: III. Supernodes and supermeshes

01/29/2019 Lecture 6.

- 6.1 Nodal analysis with an independent current source
- 6.2 Nodal analysis with voltage sources, Supernodes
- 6.3 Nodal analysis with controlled sources
- 6.4 Mesh analysis with current sources
- 6.5 Mesh analysis with controlled sources, Supermeshes



## Chapter 7

# Circuit analysis: IV. Circuit theorems

01/31/2019 Lecture 7.

**7.1 Circuit theorems**

**7.2 Linearity**

**7.3 Superposition**

**7.4 Source transformation**

**7.5 Thevenin equivalents**

**7.6 Norton equivalents**

**7.7 Equivalents with dependents**



## Chapter 8

# Circuit analysis: V. When to choose between analyses

02/05/2019 Lecture 8.



## Chapter 9

# A review of the material thus far; Homework II

02/07/2019 Lecture 9.

### 9.1 How to measure voltage and current





# Exam I

02/12/2019



# Part II

## Systems



## Chapter 10

# The Laplace Transform: I. What it is and why it is important

02/14/2019 Lecture 10.

10.1 How do we know our world looks like this?

10.2 Euler's identity / Euler's formula

10.3 The Laplace transform

10.4 The Laplace transform of 1

10.5 The  $s$ -plane

10.6 The linearity of the Laplace transform

10.7 The Laplace transform of  $e^{at}$

10.8 The Laplace transform of  $dx/dt$

10.9 The Laplace transform in RLC circuits

10.9.1 Resistors

10.9.2 Inductors

10.9.3 Capacitors

10.9.4 RLC

10.10 Two important places, zeros and poles

## Chapter 11

# The Laplace Transform: II. How to use it

02/19/2019 Lecture 11.

11.1 The inverse Laplace transform

11.2 The Laplace transform of  $\sin$

11.3 The Laplace transform of  $t^n$

11.4 Some applicability





## Chapter 12

# Circuits as ODEs: I. First-order

02/21/2019 Lecture 12.

### 12.1 Source-free RC circuits

#### 12.1.1 One resistor, one capacitor

#### 12.1.2 Two or more resistors and/or capacitors

### 12.2 Source-free “active” circuits

### 12.3 First-order systems with sources

### 12.4 Several singular functions

#### 12.4.1 Unit step function, $u(t - t_0) = 1, t > t_0$

The Laplace transform of the unit step function

#### 12.4.2 Unit impulse function, $\delta(t) = du(t)/dt$

Its “sifting” abilities

The Laplace transform of the unit impulse function

#### 12.4.3 Unit ramp function, $r(t) = \int u(t)dt$

The Laplace transform of the unit impulse function



## Chapter 13

# Circuits as ODEs: II. Second-order

02/26/2019 Lecture 13.

### 13.1 A series RLC circuit



## Chapter 14

# System response: I. Convolution; Homework III

02/28/2019 Lecture 14.

### 14.1 An introduction to thinking in systems

Viewing everything as a “system”.

#### 14.1.1 Domains of interest, of command

#### 14.1.2 The time-domain, or: our typical realm

#### 14.1.3 The frequency-domain, or: our new realm

#### 14.1.4 The $s$ -domain, or: our magical realm

### 14.2 Inputs and outputs

### 14.3 Somewhere in the between

### 14.4 Convolution in the time-domain

### 14.5 Multiplication in the frequency- and $s$ -domain



## Chapter 15

# System response: II. Stability

03/12/2019 Lecture 15.

### 15.1 An introduction

#### 15.1.1 What do we mean by stability?

### 15.2 Undamped, $\zeta = 0$

### 15.3 Underdamped, $0 < \zeta < 1$

### 15.4 Overdamped, $\zeta > 1$





# Part III

## & Signals



## Chapter 16

# System response: III. The frequency domain

03/14/2019 Lecture 16.



## Chapter 17

# System response: IV. Filters

03/19/2019 Lecture 17.



## Chapter 18

# System response: V. Feedback; Homework IV

03/21/2019 Lecture 18.





# Exam II

03/26/2019



**Part IV**

**in Biomedical Engineering**



## Chapter 19

# Bioelectricity: I. Passive properties

03/28/2019 Lecture 19.

**19.1** Modeling biological material with a simple circuit,  $R_1 + (R_2 || C)$

**19.2** Resistance-Reactance Plane

**19.3** What can we do with this information?



## Chapter 20

# Bioelectricity: II. Active properties

04/02/2019 Lecture 20.





## Chapter 21

# Bioelectricity: III. Measurement

04/04/2019 Lecture 21.



## Chapter 22

# Digital circuits: I. Discretization

04/09/2019 Lecture 22.



## Chapter 23

# Digital circuits: II. Logic; Homework V

04/11/2019 Lecture 23.



## Chapter 24

# Happenstance: A few BME specific situations

04/16/2019 Lecture 24.





## Chapter 25

# Circumstance: A few BME specific standards

04/18/2019 Lecture 25.



## Chapter 26

# A philosophy of circuits, systems, and signals; Homework VI

04/23/2019 Lecture 26.



# Exam III

04/26/2019